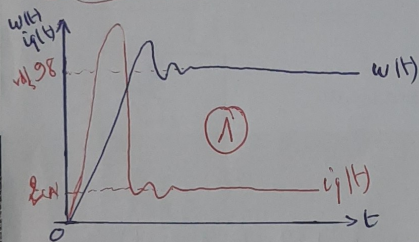


on Applique Méthode Hevosale

$$2^{\circ} \text{ HIP) } = \frac{f(0)}{F(0)} + \sum \frac{f(p_i)}{p_i F'(p_i)} e^{p_i t} \quad \begin{matrix} p_1 \\ p_2 \end{matrix}$$

$$\Rightarrow i(t) = 2 - 128 e^{-8.873t} + 126 e^{-1.127t} \quad (1.5)$$

$$w(t) = 98 + 14 e^{-8.873t} - 1251 e^{-1.127t} \quad (1.5)$$



EX2 à t=0 K ouvert

$$\begin{cases} E = (R+v)i(t) + L \frac{di(t)}{dt} \\ i = i_f + i_e \end{cases} \quad (0.5)$$

1° $i_f = ?$ $t \rightarrow \infty \rightarrow R P$

$$i_f = \frac{E}{R+v} = \frac{1}{3} \text{ A} \quad (1.5)$$

2° $Z(p)$

$$I(p) = \frac{E}{p(R+v+Lp)}$$

$$\Rightarrow p = \frac{-(R+v)}{L} = -600 \quad (1.5)$$

3° $i_e(t)$?

$$i_e(t) = A e^{pt}$$

4° condition initiale $i(0) = i(0) = ?$

$$i(0) = \frac{E}{R} \quad (0.5)$$

$$i(0) = \frac{E}{R+v} + A e^0 = \frac{E}{R}$$

$$\Rightarrow A = \frac{vE}{R(R+v)} \quad (1.5)$$


$$\Rightarrow i(t) = \frac{E}{R+v} + \frac{vE}{R(R+v)} e^{-(\frac{R+v}{L})t} \quad (1)$$

$$i(t) = \frac{1}{3} + \frac{5}{3} e^{-600t} \quad (1.5)$$

$$V_L(t) = L \frac{di(t)}{dt} = L \cdot \frac{d}{dt} \left(\frac{vE}{R(R+v)} e^{pt} \right)$$

$$V_L(t) = \frac{L \cdot vE \cdot (R+v)}{R(R+v) \cdot L} e^{pt}$$
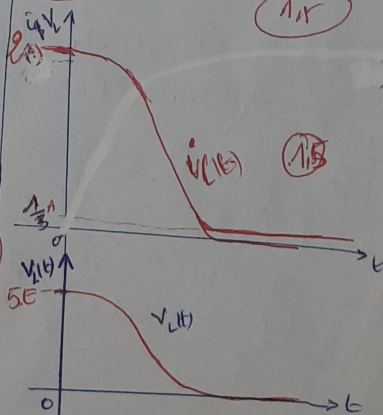
$$V_L(t) = \frac{vE}{R} e^{pt} = 5 \times 5 e^{-600t} \quad (1.5)$$



- $L_q = 0.1 \text{ H}$, $R_q = 10 \Omega$, $r = 250 \Omega$, $L = 0.5 \text{ H}$, $N = 1000$, $C_r = 2 \text{ mF}$, $\omega = 100 \text{ rad/s}$, $E = 100 \text{ V}$, $R = 50 \Omega$.
- Quelle est la loi de variation de $i_q(t)$, $\omega(t)$?
 - Trace l'allure de $i_q(t)$, $\omega(t)$?


Exercice 01 : (10 pts)

On considère le circuit suivant : $E = 100 \text{ V}$, $R = 50 \Omega$, $r = 250 \Omega$, $L = 0.5 \text{ H}$.


à $t = 0$ on ouvre K .

1. Déterminer la loi de variation de $i(t)$, $V_L(t)$?

2. Tracer l'allure $i(t)$ et $V_L(t)$?

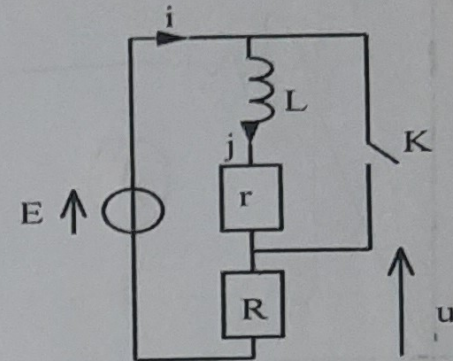

EX1 10pts

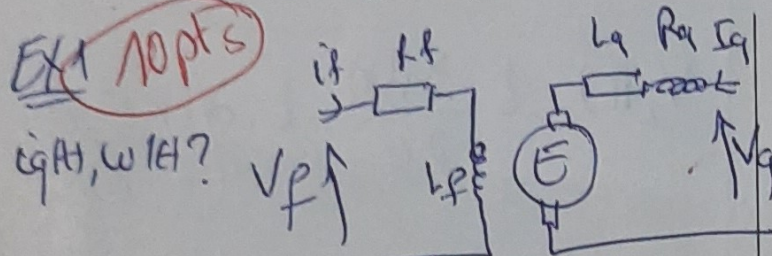

$$\begin{cases} V_g = R_q i_q + L_q \frac{di_q}{dt} \rightarrow (1) \\ V_g = R_q i_q + L_q \frac{di_q}{dt} + r i_g \rightarrow (2) \\ C_e - C_r = J \frac{d\omega}{dt} + f \cdot \omega \rightarrow (3) \end{cases}$$

APP. T.L. $\dot{e}_g(2)$ et $e_g(3)$

$$\begin{cases} \frac{V_g}{p} = (R_q + L_q p) I_q(p) + K_{gf} \omega(p) \\ -\frac{C_r}{p} = -K_{gf} I_q(p) + J p \omega(p) \end{cases}$$

$$\begin{bmatrix} \frac{V_g}{p} \\ -\frac{C_r}{p} \end{bmatrix} = \begin{bmatrix} (R_q + L_q p) & K_{gf} \\ -K_{gf} & J p \end{bmatrix} \begin{bmatrix} I_q(p) \\ \omega(p) \end{bmatrix}$$

donc, $\begin{vmatrix} R_q + L_q p & K_{gf} \\ -K_{gf} & J p \end{vmatrix}$, $\omega(p) = \frac{R_q + L_q p}{\Delta} \frac{V_g}{p}$

$$\Delta = L_q J p^2 + \frac{R_q}{J} p + \frac{K_{gf}^2}{J}$$

$$I_q(p) = \frac{\frac{V_g}{p} p + \frac{K_{gf} C_r}{L_q J}}{p \left(p^2 + \frac{R_q}{L_q} p + \frac{K_{gf}^2}{L_q J} \right)}$$

$$\omega(p) = \frac{-\left[\frac{C_r}{J} p - \frac{V_g K_{gf}}{L_q J} + \frac{C_r R_q}{L_q J} \right]}{p \left(p^2 + \frac{R_q}{L_q} p + \frac{K_{gf}^2}{L_q J} \right)}$$

$$I_q(p) = \frac{1000p + 20}{p(p^2 + 10p + 10)}$$

$$\omega(p) = \frac{-2p + 980}{p(p^2 + 10p + 10)}$$